


$$V_x = 7.5 V$$

181

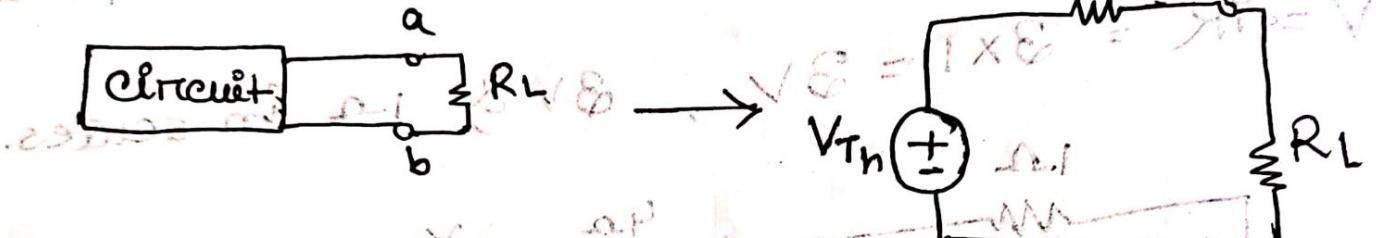
## Thevenin's theorem

object 21 & AG 2020

$$I = \frac{V}{R} = \frac{V_0 + V_{Th}}{R_{Th} + R_L}$$



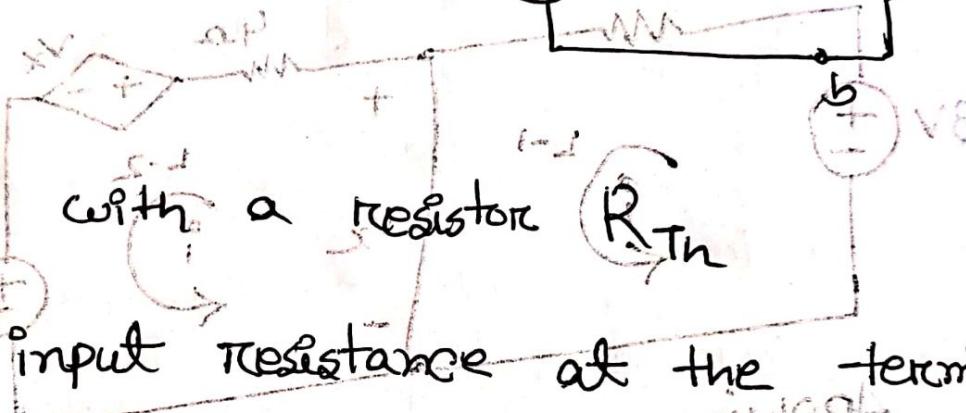
•  $V_{Th}$  in series with a resistor  $R_{Th}$  is the input resistance at the terminals when all the independent sources are turned off.



$$I = \frac{V}{R} = \frac{V}{R_{Th} + R_L}$$

**Example → 4.8**

NTV Freshers

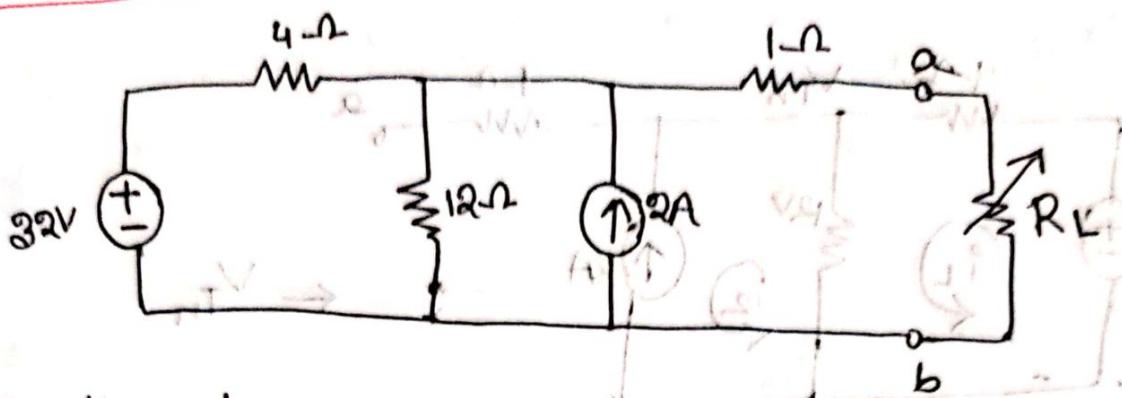


Find the Thevenin equivalent circuit of the circuit to the left of the terminals a-b, then find the current through  $R_L = 6 \Omega$ .

SOL

We find  $R_{Th}$  by turning off 32V (replace it in an open short circuit) & 2A (replace it in an open circuit). [Other methods]

Finding  $R_{Th}$

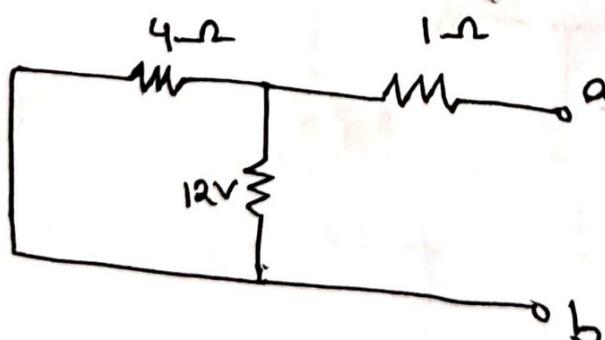

Hence, 12V & 4Ω in parallel.


$$R_{Th} = \left( \frac{1}{4} + \frac{1}{12} \right)^{-1} + 1$$

● ● ○ ○ = 4Ω  
REDMI NOTE 10

VOE = NTV

## Finding $V_{Th}$

8.13 - 34

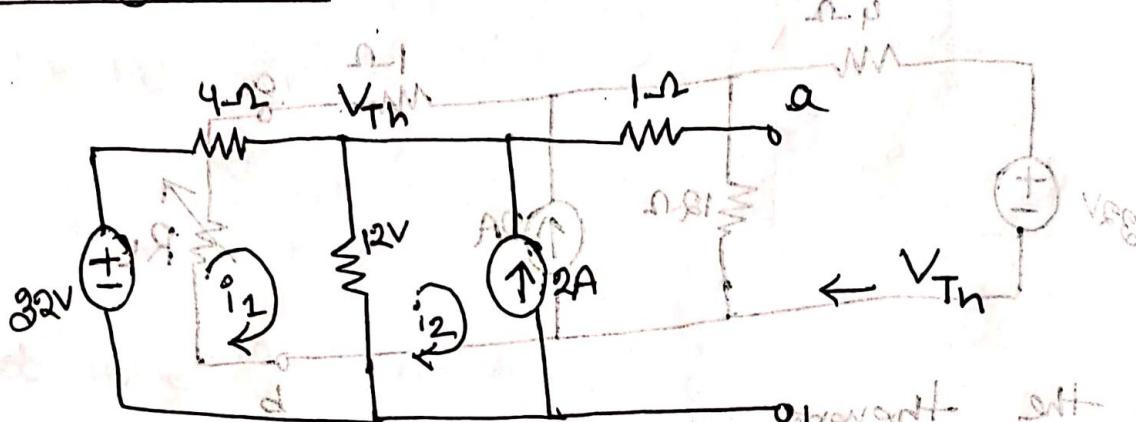

we apply mesh analysis. in L-1, d-s elements

$$-32 + 4i_1 + 12i_1 - 12i_2 = 0$$

$$\Rightarrow 16i_1 - 12i_2 = 32$$

in L-2,

$$i_2 = -2 \text{ A}$$


[As direction negative]

Put value of  $i_2$  in eq ①

$$16i_1 - 12(-2) = 32$$


$$\Rightarrow 16i_1 = 8$$

$$\therefore i_1 = 0.5 \text{ A}$$

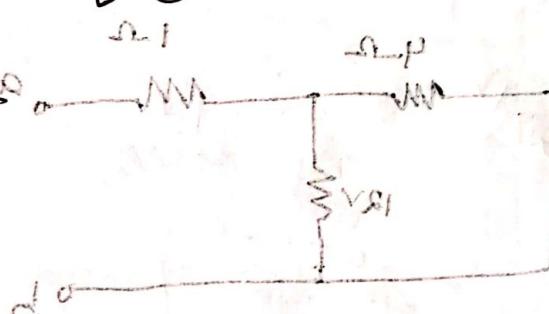

$$\text{Now, } V_{Th} = 12i_1 - 12i_2 = 12(0.5 + 2) = 30 \text{ V}$$

# Thevenin equivalent circuit

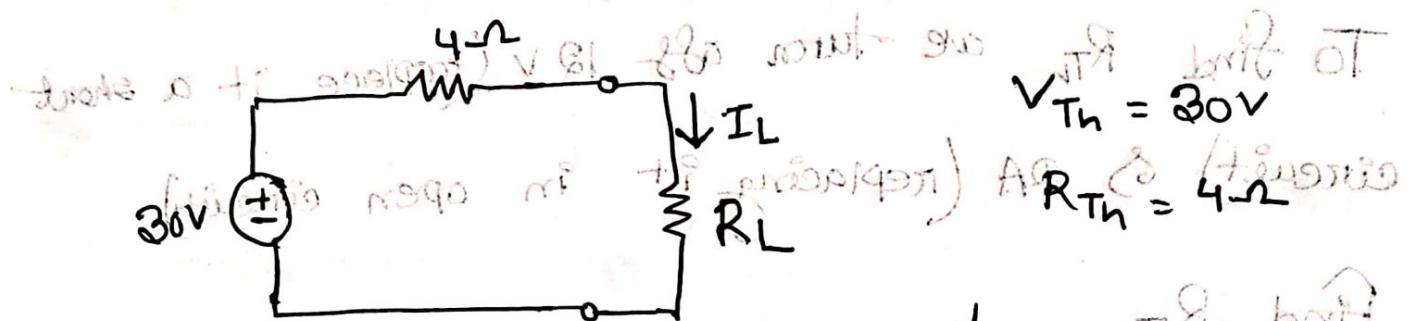

Current,


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

when  $R_L = 6\Omega$   $\rightarrow I_L = \frac{30}{4+6} = 3A$

$R_L = 16\Omega$ ,  $I_L = \frac{30}{4+16} = 1.5A$

$R_L = 36\Omega$ ,  $I_L = \frac{30}{4+36} = 0.75A$

## Practice Problem $\rightarrow 4.8$

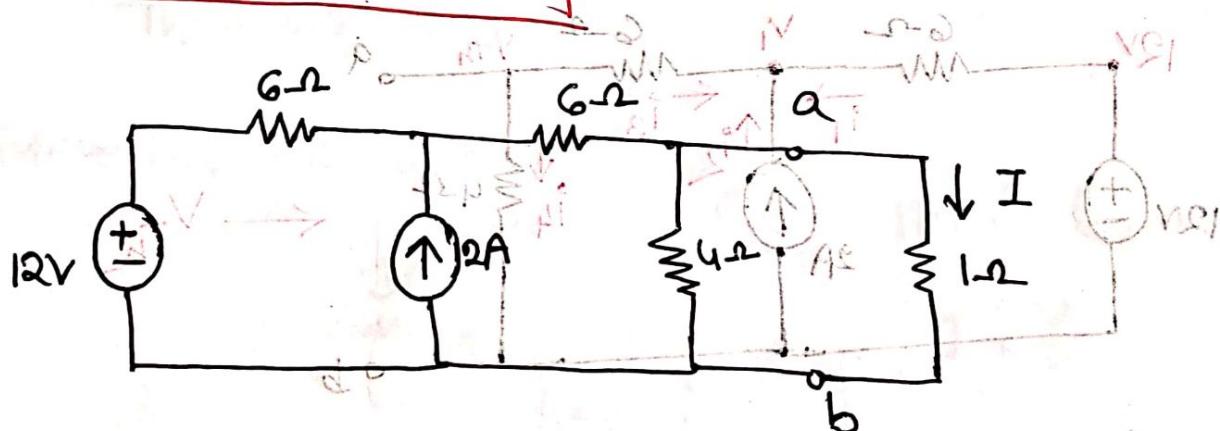

Using Thevenin's theorem, find equivalent circuit to the left of the terminals, then find  $I$ .


$$\theta = \varepsilon^1 + \delta^1 + \gamma^1$$



SOL

To find  $R_{Th}$ , we turn off 12V (replace it a short circuit) & 2A (replacing it in open circuit)


Find  $R_{Th}$

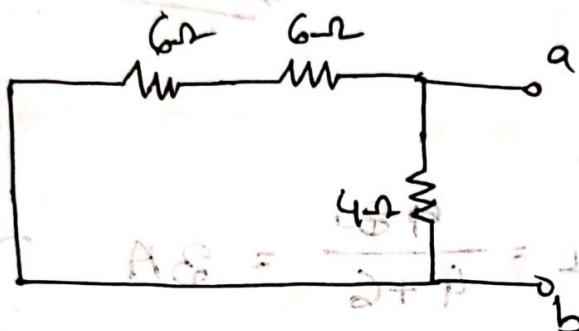

$$6\Omega + 6\Omega = 12 - 2I \quad \text{or} \quad 2I = 12$$

$$R_{Th} = \left( \frac{1}{12} + \frac{1}{4} \right)^{-1} = 3\Omega$$

Find  $V_{Th}$

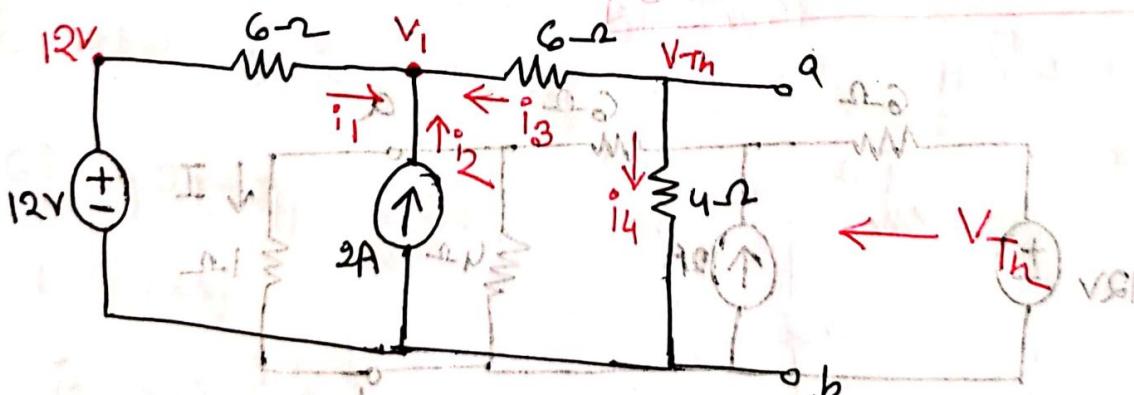

By Applying Node Analysis

at node - 1,

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{12 - V_1}{6} + 2 + \frac{V_{Th} - V_1}{6} = 0$$

$$\Rightarrow \frac{12 - V_1 + 12 + V_{Th} - V_1}{6} = 0$$

$\therefore -2V_1 + V_{Th} = -24 \quad \text{--- (1)}$

Similarly we get three equations for three nodes.

At node 2,


$$i_3 + i_4 = 0$$

$$\Rightarrow \frac{V_{Th} - V_1}{6} + \frac{V_{Th}}{4} = 0$$


$$\Rightarrow \frac{2V_{Th} - 2V_1 + 8V_{Th}}{12} = 0$$

$$\Rightarrow \boxed{-2V_1 + 14V_{Th} = 0} \quad \text{--- (2)}$$

Solving (1) & (2)

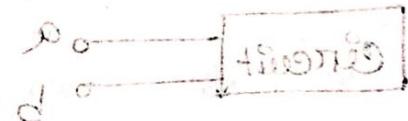

Thevenin's equivalent circuit

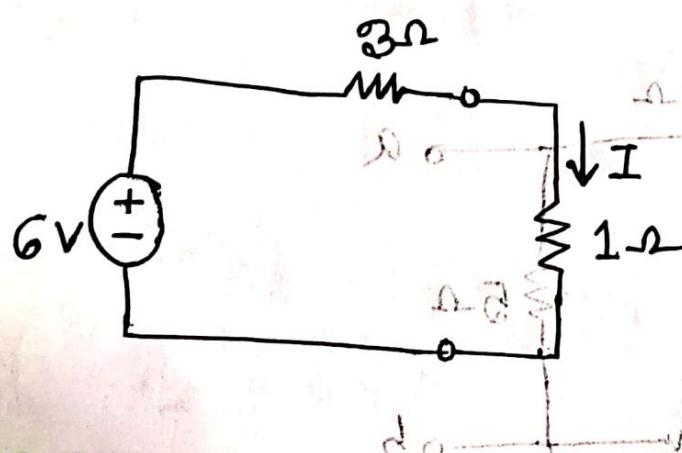

$$I = \frac{V}{R}$$

$$= \frac{6}{3+1}$$

$$I = 1.5A$$

*An*



REDMI NOTE 10



## Norton's theorem

- Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source.
- $I_N$  in parallel with a resistor  $R_N$
- $R_N$  is the "input resistance" when all the sources are turned off.


As,

$$R_N = R_{Th}$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

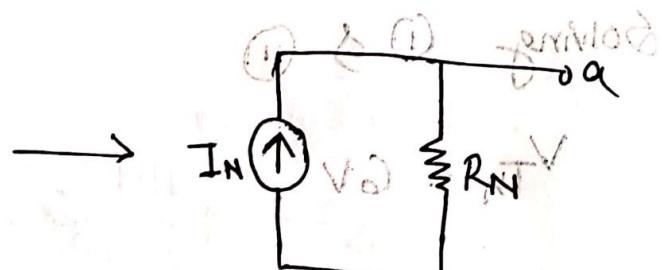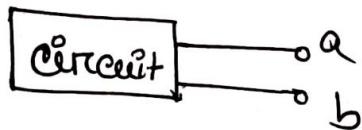

Example → 4.11

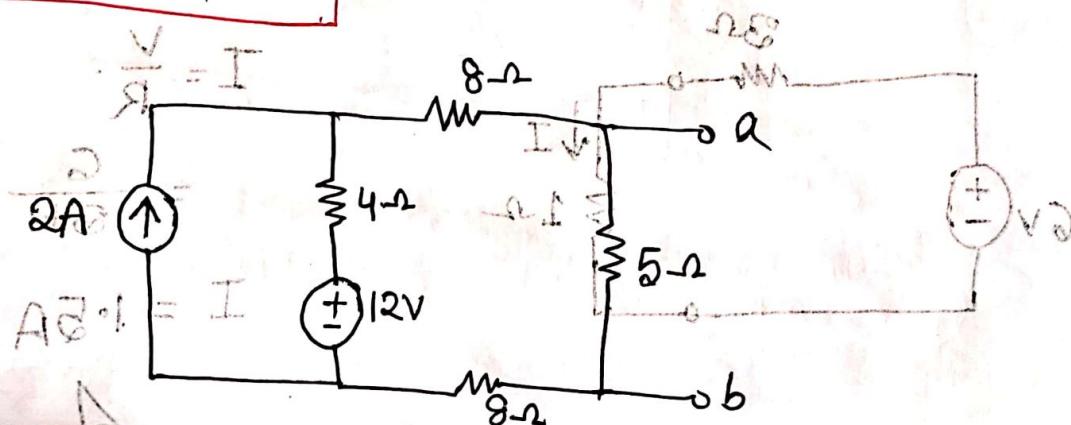


Find Norton equivalent circuit in terminals a-b

Sol ↗

To find  $R_{Th}$  return off  $2A$  &  $12V$  =  $\text{mV}$


Find  $R_{Th}$

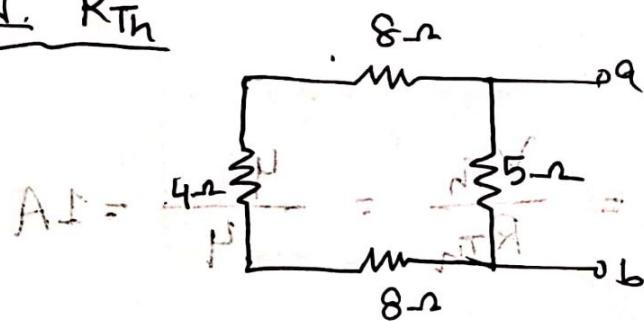

$$V_P = \text{mV} \leftarrow$$

$$R_{Th} = \left( \frac{12 - P}{8 + 4 + 8} + \frac{12}{5} \right)^{-1} = 4 \Omega$$

Find  $V_{Th}$

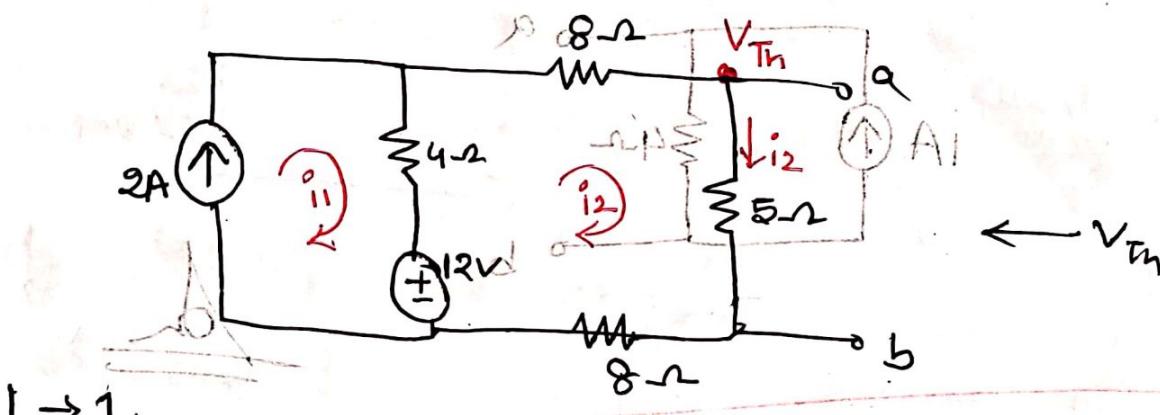

$L \rightarrow 1,$

$$i_1 = 2A$$

in  $L \rightarrow 2,$

$$4i_2 + 8i_2 + 5i_2 + 8i_2 - 12 - 4i_1 = 0$$

$$\Rightarrow 25i_2 - 4 \times 2 = 12$$

$$\Rightarrow 25i_2 = 20$$

current  $i_2 = 0.8A$




$$V_{Th} = i_2 \times 5 = 0.8 \times 5$$

$$\Rightarrow V_{Th} = 4V$$

As we know,  $I_N = \frac{V_{Th}}{R_{Th}} = \frac{4}{4} = 1A$


$$R_N = R_{Th} = \frac{4\Omega}{8+4\Omega} = 1\Omega$$

Norton equivalent circuit.

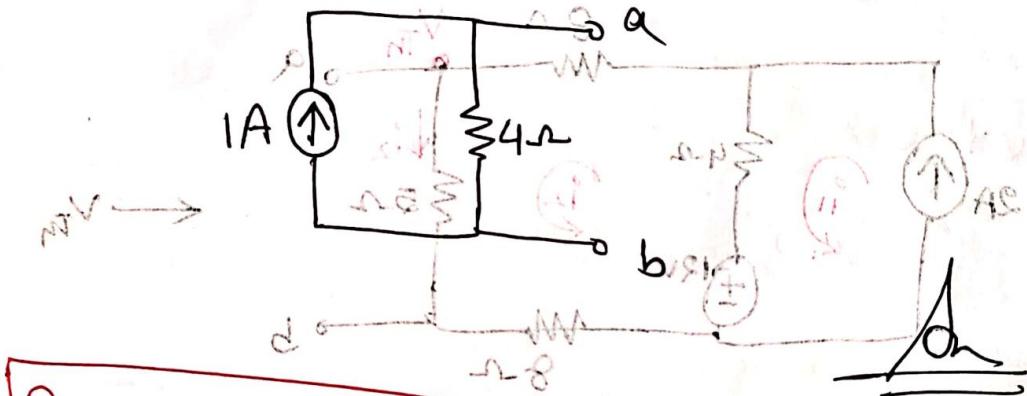

Practice Problem  $\rightarrow$  4.11

$$AS = ?$$

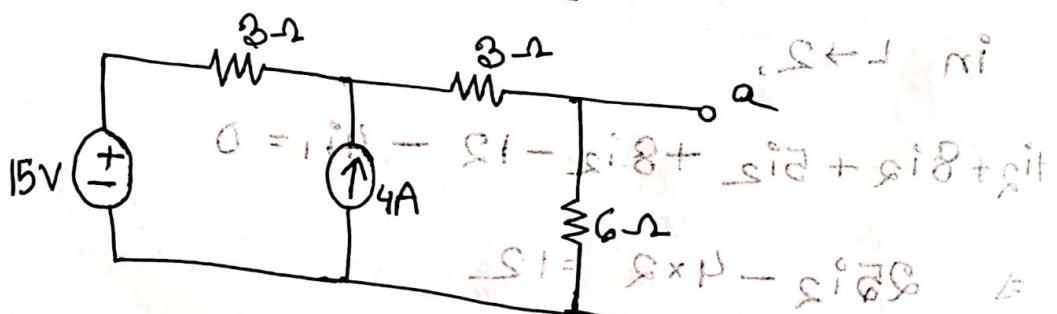

Find the Norton's equivalent circuit at terminals a-b.


$$AS = ?$$



Sol. To find  $R_{Th}$  turn off 15V & 4A.


$$0 = i_1 + \frac{V}{R}$$

Find  $R_{Th}$

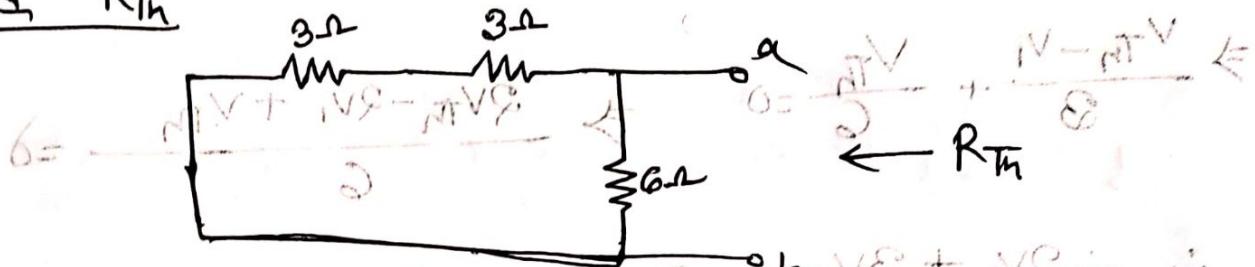

$$R_{Th} = \left( \frac{1}{3+3} + \frac{1}{6} \right)^{-1} = 3\Omega$$

Find  $V_{Th}$

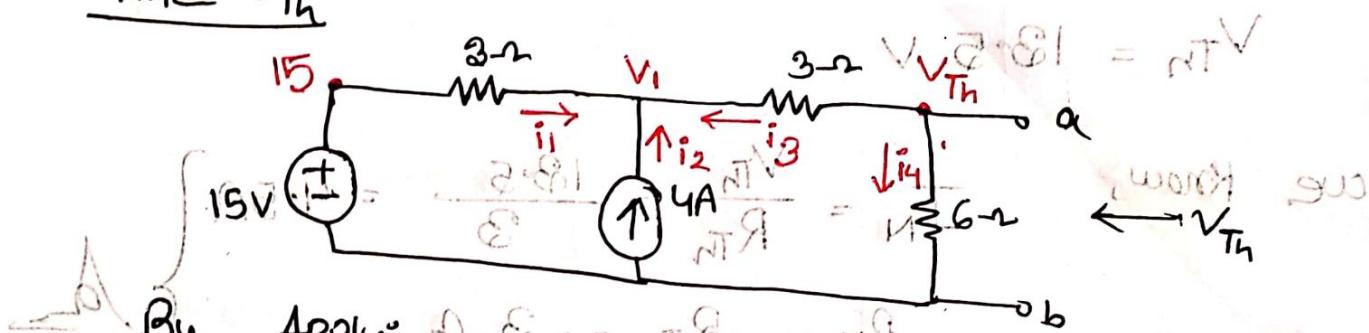

By Applying Node Analysis,


at node 1,

Hence the voltage across

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{15 - V_1}{3} + 4 + \frac{V_{Th} - V_1}{3} = 0$$
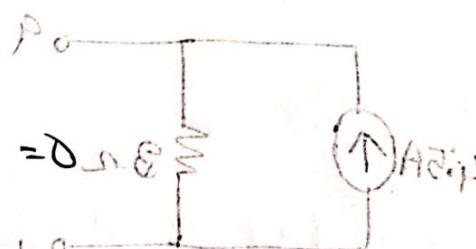
$$\Rightarrow \frac{15 - V_1 + 12 + V_{Th} - V_1}{3} = 0$$



$$\therefore -2V_1 + V_{Th} = -27 \quad \text{--- (1)}$$

At node 2

$$i_3 + i_4 = 0$$

$$\Rightarrow \frac{V_{Th} - V_1}{3} + \frac{V_{Th}}{6} = 0 \Rightarrow \frac{2V_{Th} - 2V_1 + V_{Th}}{6} = 0$$

$$\therefore -2V_1 + 3V_{Th} = 0$$

Solving ① & ⑪

$$V_{Th} = 13.5 \text{ V}$$

we know,

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{13.5}{3} = 4.5 \text{ A}$$

$$R_N = R_{Th} = 3 \Omega$$

Norton equivalent circuit



$$0 = e_i + v_o + i_o$$


$$0 = \frac{13.5 - \text{RTV}}{6} + 0 + \frac{13.5 - \text{RTV}}{3}$$

$$0 = \frac{13.5 - \text{RTV}}{6} - \frac{13.5 - \text{RTV}}{3}$$

$$0 \rightarrow \text{RTV} = \text{RTV} + \text{RTV} - \therefore$$
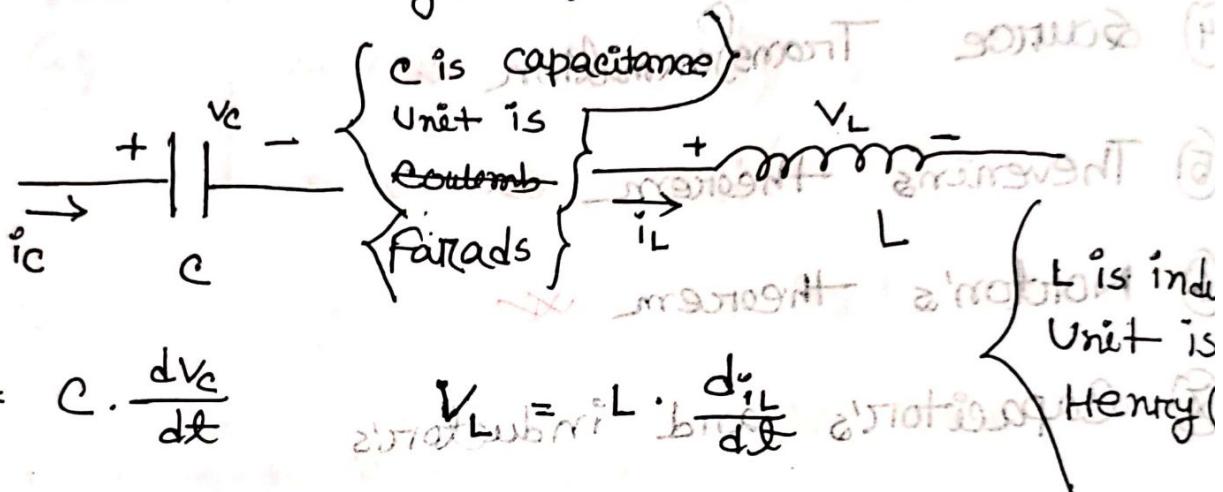
## Capacitors and inductors

- \* Resistor is an energy dissipating element.
- \* Capacitors are energy storing elements.
- \* Inductors hold magnet field (current)




- \* In a DC circuit  $i_A = \frac{V_C}{C}$

Capacitors behaves as open circuit  $\downarrow$  capacitance voltage


Inductors behaves as short circuit

- \* Series and parallel capacitors

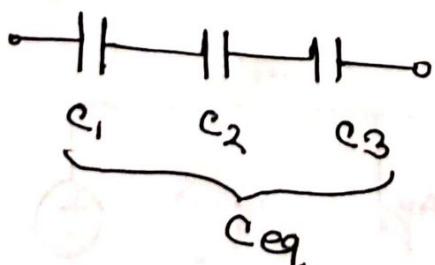


$$C_{eq} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

equivalent circuit diagram

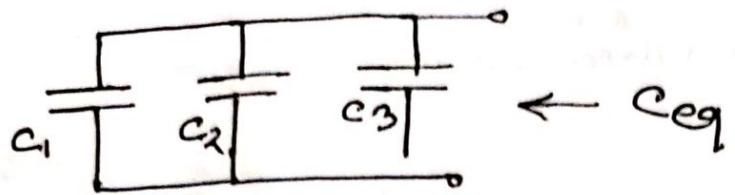


$$C_{eq} = C_1 + C_2 + C_3$$

### \* Series and Parallel inductors

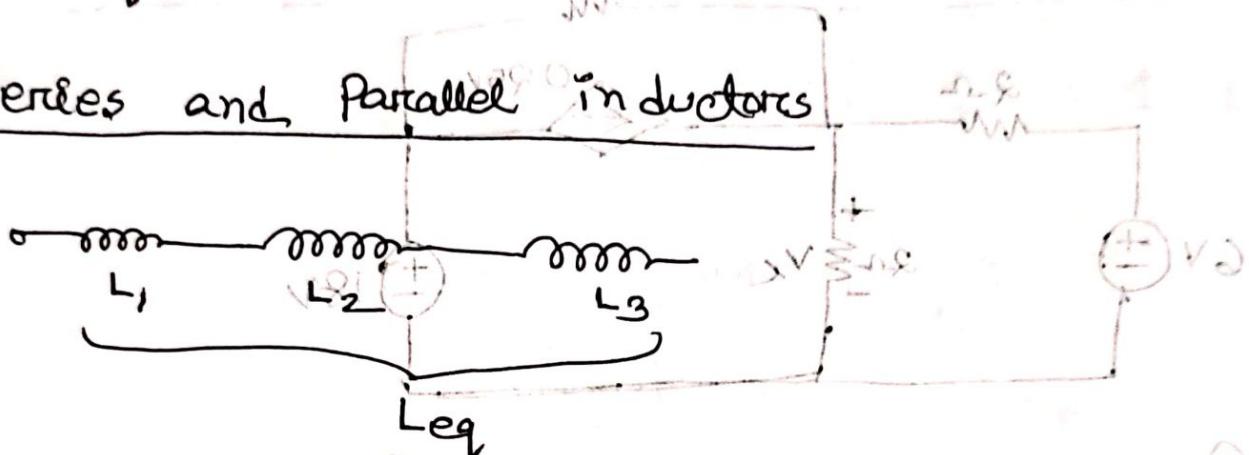

$$L_{eq} = L_1 + L_2 + L_3$$

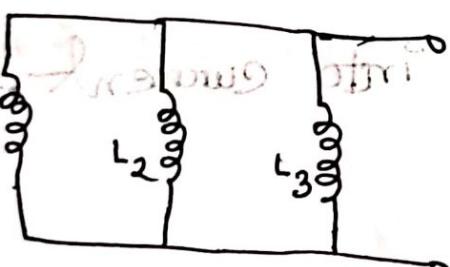

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$

$$L_{eq} = \left( \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)^{-1}$$

- A capacitor consists of two parallel conducting plates separated by an insulator.
- An inductor consists of a coil of conducting wires.



# Capacitors & Inductors

## Capacitors

in series.


$$C_{eq} = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$

$$C_{eq} = C_1 + C_2$$

## Inductors


in series

$$L_{eq} = L_1 + L_2$$

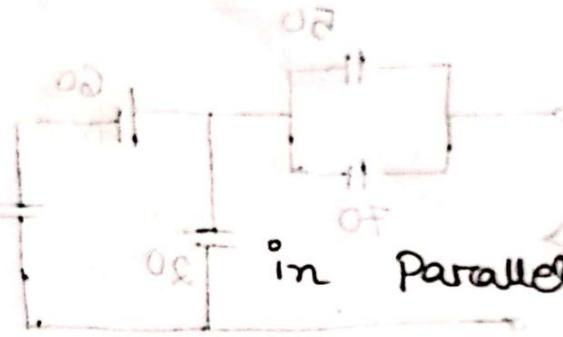

$$L_{eq} = \left( \frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$

### Example → 6.6

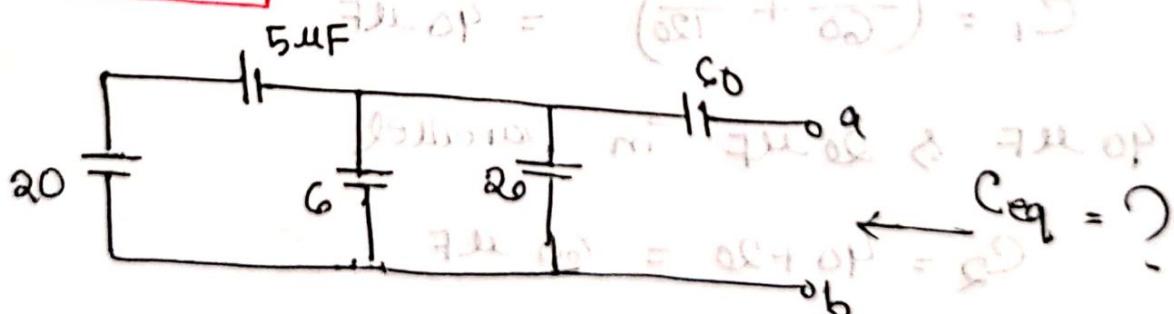

Here, 20 μF & 5 μF in series & then in parallel

$$C_{1,2} = \left( \frac{1}{20} + \frac{1}{5} \right)^{-1} = 4 \mu F$$

$$4 \mu F, 6 \mu F, 20 \mu F \text{ in parallel}$$

$$C_{eq} = \left( \frac{1}{20} + \frac{1}{6} + \frac{1}{4} \right)^{-1} = 2.5 \mu F$$


$$C_2 = 4 + 6 + 20 = 30 \mu F$$

$30 \mu F$  &  $60 \mu F$  in series.

$$C_{eq} = \left( \frac{1}{30} + \frac{1}{60} \right)^{-1} = 20 \mu F$$

Practice Problem  $\rightarrow$  Q. 6
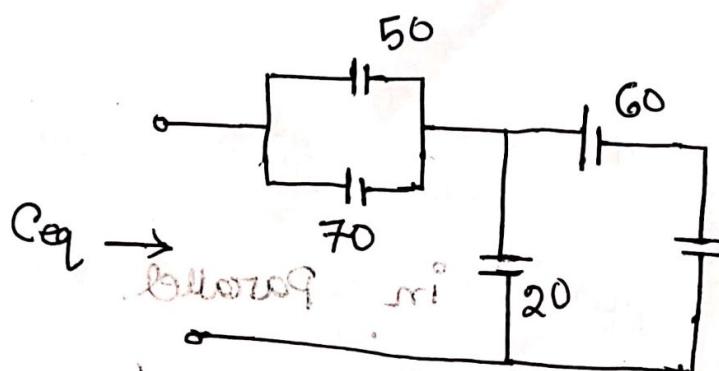
$$\left( \frac{1}{25} + \frac{1}{15} \right) = ?$$



$$C_{eq} \rightarrow \text{Follow me} \quad 120 \mu F \quad C_{eq} \text{ is?}$$

$$\left( \frac{1}{25} + \frac{1}{15} \right) = ?$$

$$C_1 = \left( \frac{1}{60} + \frac{1}{120} \right)^{-1} = 40 \mu F$$

$40 \mu F$  &  $20 \mu F$  in parallel

$$C = \frac{1}{\frac{1}{40} + \frac{1}{20}} = 120 \mu F$$

$50 \mu F$  &  $70 \mu F$  in parallel

$$C_2 = 50 + 70 = 120 \mu F$$

$$C_2 \text{ & } C_3 (60 \mu F \text{ & } 120 \mu F) \text{ in series.}$$

$$C_{eq} = \left( \frac{1}{60} + \frac{1}{120} \right)^{-1} = 40 \mu F$$

## Inductors


in series

$$L_{eq} = L_1 + L_2$$

in parallel

$$L_{eq} = \left( \frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$

Example → G.11

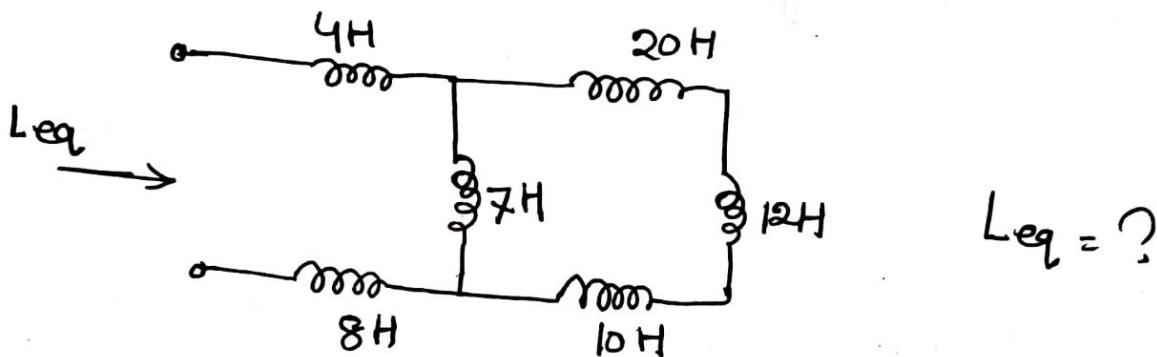

Sol.

20H, 12H, 10H in series.

$$L_1 = 20 + 12 + 10 = 42 \text{ H}$$

42H & 7H in parallel

$$L_2 = \left( \frac{1}{42} + \frac{1}{7} \right)^{-1} = 6 \text{ H}$$

4H, 6H & 8H in series.

$$L_{eq} = 4 + 6 + 8 = 18 \text{ H}$$

Ans

## \* Difference between AC & DC Power

AC (Alternating Current)

$$I = \left( \frac{1}{R} + \frac{1}{X_L} \right) = \frac{V}{Z}$$

DC (Direct Current)

$$I = \frac{V}{R}$$

(i) Current changes its direction.

(i) Current doesn't change its direction

(ii) Capacitors & inductors work as impedance

(ii) Capacitors behave like an open circuit, Inductor behave like a short circuit

(iii) Has complex power. Thus contains imaginary part

(iii) Doesn't contain any imaginary part only containing real part


(iv) Used in conventional power supply.

Ex → (Refrigerator, Fan, AC)

$I^2(R + j(X_L - X_C)) = S$

(iv) Used in conventional household electronics

Ex → (Mobile, Laptop).

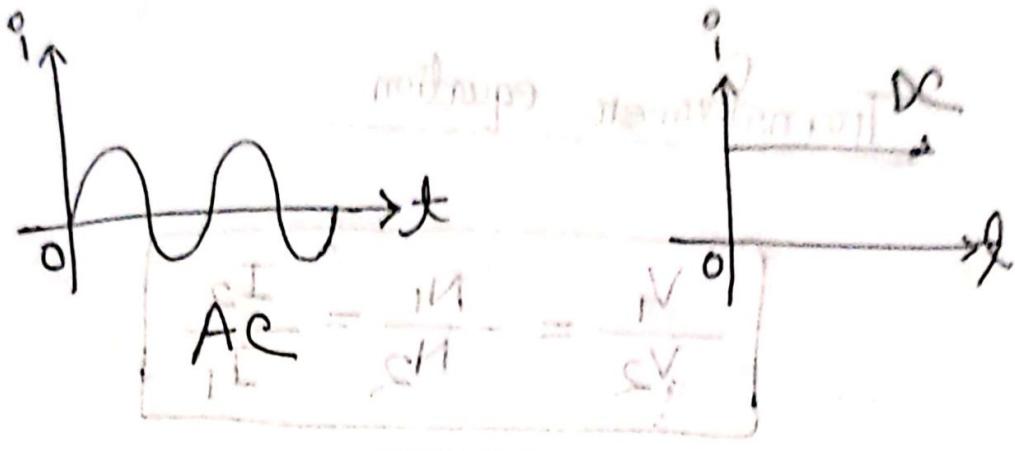


## Transformers.

One level AC  $\rightarrow$  Another level AC

Definition:  $V_1 = V_2 \Leftarrow$

An apparatus for reducing or increasing the voltage of an alternating current.

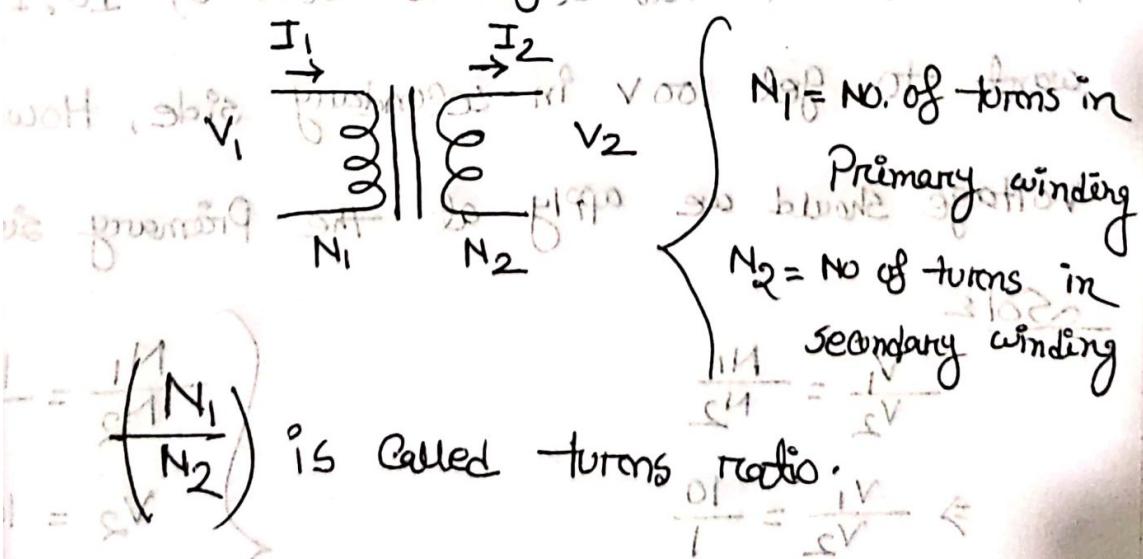\* Transformer is used to step up or step down AC voltage.



$$T = \frac{N_1}{N_2}$$

is called turns ratio.

$$T = \frac{V_1}{V_2}$$

$$V_{\text{output}} = T \times V_{\text{input}} = V_1 \Leftarrow$$

## Transformer equation

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\therefore \frac{V_1 I_1}{V_2 I_2} = 1$$

OA level  $\Rightarrow V_1 I_1 = V_2 I_2$  level OAO

$$\Rightarrow P_1 = P_2 \quad \text{notifiable}$$

generator side power not analogous to  
load side power and  
Primary side Power in the  
Secondary side Power in the

Problem up side of base of transformer \*

A transformer has a ~~option~~ ratio of 10:1. If we want to get 100 V in secondary side, How much voltage should we apply at the primary side?

Sol:  $\frac{V_1}{V_2} = \frac{N_1}{N_2}$

$$\Rightarrow \frac{V_1}{V_2} = \frac{10}{1}$$

$$\Rightarrow V_1 = 100 \times 10 = 1000 V$$

$$\left\{ \begin{array}{l} \frac{N_1}{N_2} = \frac{10}{1} \\ V_2 = 100 V \end{array} \right.$$

$$V_1 = ?$$